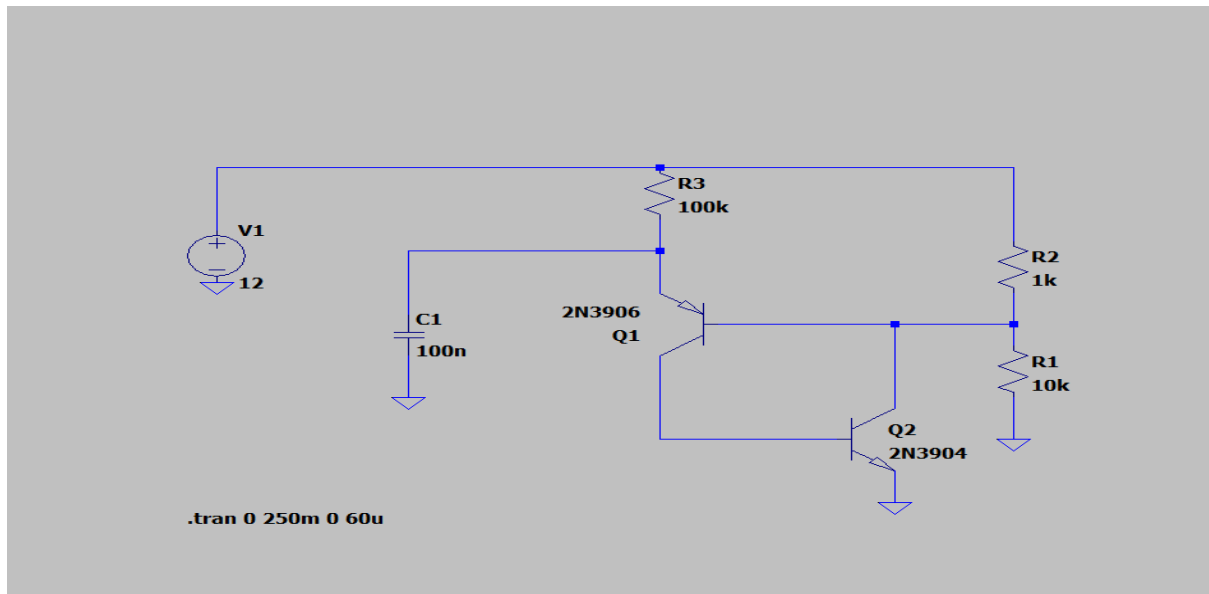


EXPERIMENT – 5

DESIGN AND SIMULATION OF UJT RELAXATION OSCILLATOR USING LTSPICE

LTspice Diagram



Graph

